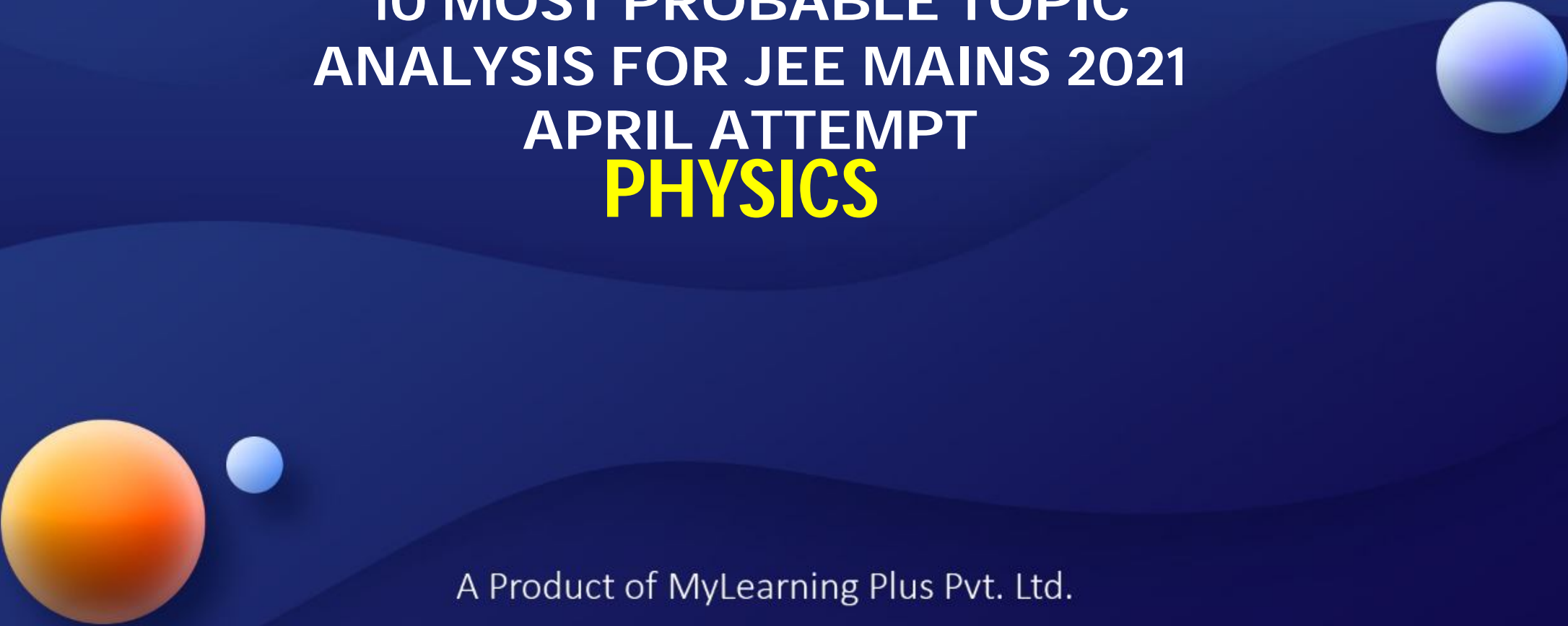


10 MOST PROBABLE TOPIC  
ANALYSIS FOR JEE MAINS 2021  
APRIL ATTEMPT  
**PHYSICS**



A Product of MyLearning Plus Pvt. Ltd.

Feb-21

March-21

Topic Name

P-N JUNCTION DIODE

Chapter Name

SEMICONDUCTOR  
ELECTRONICS:  
MATERIALS, DEVICES  
AND SIMPLE CIRCUITS

Topic Name

P-N JUNCTION DIODE


Total Questions

05

Total Questions

01

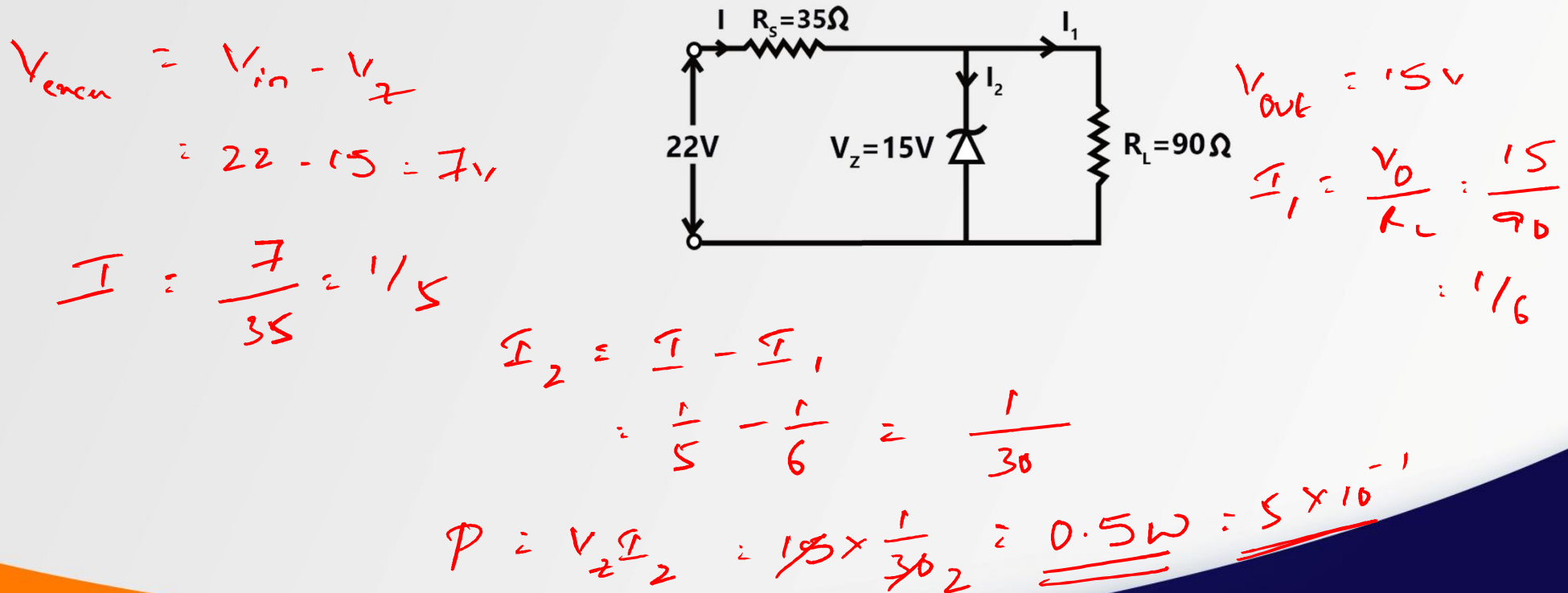1. The value of power dissipated across the zener diode ( $V_z = 15\text{ V}$ ) connected in the circuit as shown in the figure is  $x \times 10^{-1}$  watt. The value of  $x$ , to the nearest integer, is \_\_\_\_\_.



Feb-21

March-21

Topic Name

Topic Name

TRANSISTORS

TRANSISTORS

Chapter Name

SEMICONDUCTOR  
ELECTRONICS:  
MATERIALS, DEVICES  
AND SIMPLE CIRCUITS

Total Questions  
02

Total Questions  
03

2. In a transistor if increase in emitter current  $\Delta I_E$  is 4 mA and corresponding increase in collector current is 3.5 mA. Find  $\beta$

(A) 0.875

(B) 0.5

~~(C) 7~~

(D) 1

$\Delta I_C$

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$I_E = I_C + I_B$$

$$I_B = I_E - I_C = 4 - 3.5 = 0.5 \text{ mA}$$

$$\beta = \frac{3.5}{0.5} = 7$$

Feb-21

~~March-21~~

Topic Name

DIGITAL ELECTRONICS  
(LOGIC GATES)

Topic Name

DIGITAL ELECTRONICS  
(LOGIC GATES)

Chapter Name

SEMICONDUCTOR  
ELECTRONICS:  
MATERIALS, DEVICES  
AND SIMPLE CIRCUITS


Total Questions

03

Total Questions

04

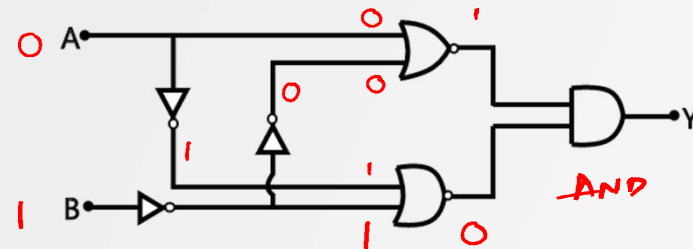3. In the logic circuit shown in the figure, if input A and B are 0 to 1 respectively, the output at Y would be 'x'. The value of x is \_\_\_\_\_.



$$\overline{A+B}$$

AND  $Y = AB$   
 $= 1 \cdot 0 = 0$



Feb-21

March-21

Topic Name

Chapter Name

Topic Name

POWER IN AC  
CIRCUIT: THE POWER  
FACTOR

ALTERNATING  
CURRENT

POWER IN AC  
CIRCUIT: THE POWER  
FACTOR

Total Questions  
01

Total Questions  
01



4. In a series LCR circuit, the inductive reactance ( $X_L$ ) is  $10\ \Omega$  and the capacitive reactance ( $X_C$ ) is  $4\ \Omega$ . The resistance ( $R$ ) in the circuit is  $6\ \Omega$ . The power factor of the circuit is :

(A)  $\frac{1}{2}$


(B)  $\frac{1}{2\sqrt{2}}$

~~(C)  $\frac{1}{\sqrt{2}}$~~

(D)  $\frac{\sqrt{3}}{2}$

$$\begin{aligned}
 Z &= \sqrt{R^2 + (X_L - X_C)^2} \\
 &= \sqrt{6^2 + (10 - 4)^2} \\
 &= 6\sqrt{2}
 \end{aligned}$$

$$\text{P.F.} = \cos\phi = \frac{R}{Z}$$

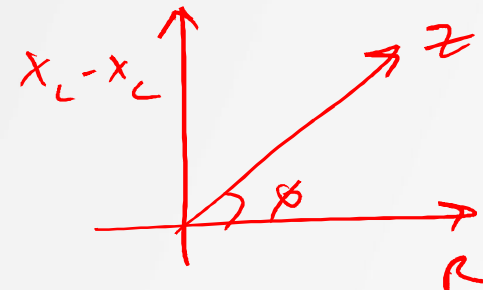

$$\cos\phi = \frac{6}{6\sqrt{2}} = \frac{1}{\sqrt{2}}$$

Feb-21

March-21

Topic Name

TRANSFORMER  
AND LC  
OSCILLATIONS

Chapter Name

ALTERNATING  
CURRENT

Topic Name


TRANSFORMER  
AND LC  
OSCILLATIONS

Total Questions  
03

Total Questions  
03

5. Find values of L and C? (All given values are RMS)

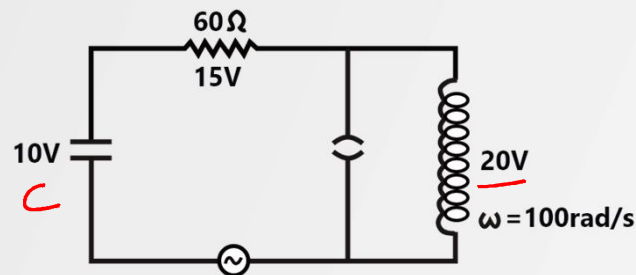- (A) 0.8 H, 500  $\mu$ F
- (B) 0.8 H, 250  $\mu$ F
- (C) 0.4 H, 250  $\mu$ F
- (D) 1.33 H, 500  $\mu$ F



$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = \sqrt{15^2 + (20 - 10)^2}$$

$$= \sqrt{15^2 + 10^2}$$

$$i = \frac{V_R}{R} = \frac{15}{60} = \frac{1}{4} \text{ A}$$

$$X_L = \omega L$$

$$V_L = i X_L \Rightarrow 20 = \frac{1}{4} [\omega L]$$

$$80 = 100 \times L$$

$$L = \frac{80}{100} = 0.8 \text{ H}$$

$$Z = \frac{V}{i} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_C = \frac{1}{\omega C}$$

$$C = 500 \mu\text{F}$$

~~Feb-21~~

~~March-21~~

Topic Name

Chapter Name

Topic Name

REPRESENTATION  
OF AC CURRENT  
AND VOLTAGE BY

ALTERNATING  
CURRENT

REPRESENTATION  
OF AC CURRENT  
AND VOLTAGE BY

Total Questions  
~~01~~

Total Questions  
~~01~~

6. The current flowing in a wire is given as  $I = I_1 \sin \omega t + I_2$ . Find the rms value of current?

(A)  $\frac{(I_1^2 + I_2^2)^{1/2}}{\sqrt{2}}$

(B)  $\frac{(I_1^2 + I_2^2)^{1/2}}{2}$

(C)  $\frac{(I_1^2 - I_2^2)^{1/2}}{\sqrt{2}}$

(D)  $\frac{(I_1^2 - I_2^2)^{1/2}}{2}$

$$I_{rms}^2 = \frac{\int I^2 dt}{\int dt}$$

$$I_{rms}^2 = \frac{(I_1^2 + I_2^2)}{2}$$

$$= \frac{(I_1^2 + I_2^2)^{1/2}}{\sqrt{2}}$$

Feb-21

March-21

Chapter Name

Topic Name

ATOMS

BOHR'S ATOMIC MODEL,  
HYDROGEN SPECTRA AND  
ATOMIC EXCITATIONS BY  
COLLISIONS

Topic Name  
BOHR'S ATOMIC MODEL,  
HYDROGEN SPECTRA AND  
ATOMIC EXCITATIONS BY  
COLLISIONS

Total Questions  
04

Total Questions  
01

7. H-atom is free to move and its electron is in state  $n = 5$ . Find recoil speed of atom when electron jumps from  $n = 5$  to  $n = 1$

- ~~(A)~~ 4.35 m/sec
- (B) 1.2 m/sec
- (C) 13.06 m/sec
- (D) 0.435 m/sec

$$E = (13.6) \left[ \frac{1}{n_1^2} - \frac{1}{n_2^2} \right] \text{ eV}$$

$$= 13.6 \left[ \frac{1}{1^2} - \frac{1}{5^2} \right] = 13.6 \left[ \frac{24}{25} \right]$$

~~CCPA~~

$$E = E_{\text{atom}} = \frac{1}{2} mv^2$$



Feb-21

March-21

Chapter Name

Topic Name

THE LINE SPECTRA OF  
THE HYDROGEN ATOM

ATOMS

Topic Name

THE LINE SPECTRA OF  
THE HYDROGEN ATOM

Total Questions  
04

Total Questions  
02

8. The first three spectral lines of H-atom in the Balmer series are given  $\lambda_1, \lambda_2, \lambda_3$  considering the Bohr atomic model, the wave lengths of first and third spectral lines  $\left(\frac{\lambda_1}{\lambda_3}\right)$  are related by a factor of approximately  $x \times 10^{-1}$ . The value of  $x$ , to the nearest integer, is \_\_\_\_\_.

\_\_\_\_\_

$$\frac{\lambda_1}{\lambda_3} = 15$$

$$\frac{1}{\lambda_1} = R \left[ \frac{1}{2^2} - \frac{1}{3^2} \right] \quad \frac{1}{\lambda_2} = R \left[ \frac{1}{2^2} - \frac{1}{4^2} \right]$$

$$\frac{1}{\lambda_3} = R \left[ \frac{1}{2^2} - \frac{1}{5^2} \right]$$

Feb-21

March-21

Chapter Name

**CURRENT ELECTRICITY**

Topic Name

**WHEATSTONE BRIDGE  
AND METERBRIDGE**

Topic Name


**WHEATSTONE BRIDGE  
AND METERBRIDGE**

**Total Questions**  
**01**

**Total Questions**  
**02**

9. The four arms of a Wheatstone bridge have resistances as shown in the figure. A galvanometer of  $15\ \Omega$  resistance is connected across BD. Calculate the current through the galvanometer when a potential difference of  $10\text{V}$  is maintained across AC.

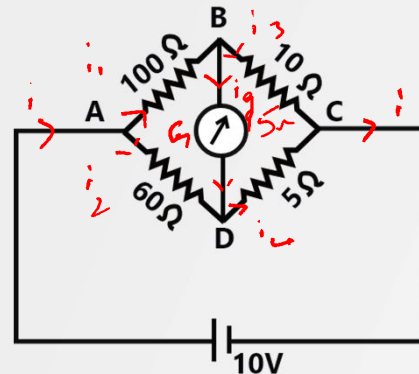- (A)  $2.44\ \mu\text{A}$
- (B)  $2.44\ \text{mA}$
- ~~(C)  $4.87\ \text{mA}$~~
- (D)  $4.87\ \mu\text{A}$



KVL ABDA

$$-i_1(100) - i_g(15) + i_2(60) = 0 \quad \text{--- (1)}$$

B C D B

$$-i_3(10) + i_4(5) + i_g(15) = 0 \quad \text{--- (2)}$$

at A

$$i = i_1 + i_2 \quad \text{--- (3)}$$

at B

$$i_1 = i_3 + i_g \quad \text{--- (4)}$$

at D

$$i_2 + i_g = i_4 \quad \text{--- (5)}$$

A S C A

$$-i_1(100) - i_3(10) + 10 = 0 \quad \text{--- (7)}$$

A D C A

$$-i_2(60) - i_4(5) + 10 = 0 \quad \text{--- (8)}$$

Feb-21

March-21

Chapter Name

Topic Name

RESISTIVITY OF VARIOUS MATERIALS

CURRENT ELECTRICITY

Topic Name

RESISTIVITY OF VARIOUS MATERIALS

Total Questions  
01

Total Questions  
01

10. A resistor of length "l" is stretched by 25 %. Find % change in its resistance?

~~(A) 56 %~~

(B) 50 %

(C) 60 %

(D) 40 %

$$R = \frac{\rho l}{A} = \frac{\rho l}{\frac{V}{l}} = \frac{\rho l^2}{V}$$

$V \rightarrow$  Volume

$$R \propto l^2$$

$$l_1 = l ; l_2 = \frac{125}{100} l_1$$

$$\frac{R_2}{R_1} = \left( \frac{l_2}{l_1} \right)^2 = \left( \frac{125}{100} \right)^2 = \frac{25}{16} \Rightarrow R_2 = \frac{25}{16} R_1$$

$$\frac{R_2 - R_1}{R_1} \times 100 = \frac{\frac{25}{16} R_1 - R_1}{R_1} \times 100 = \underline{\underline{56\%}}$$